

# Unit-3 Test

Total 6 Questions are there and each question is compulsory

...

Hi HARITDHEER, when you submit this form, the owner will be able to see your name and email address.

\* Required

1. Write your name \*

Harit Dheer

2. Write your roll no.( e.g. 01-ECEA-21) \*

40-ECEA-21

3. Class \*

☒ ECE A

☐ ECE B

4. Explain Base width modulation in BJT.(3 Marks)

As the collector voltage  $V_{CC}$  is made to increase the reverse bias, the space charge width between collector and base tends to increase, with the result that the effective width of the base decreases. This dependency of base width on collector-to-base voltage is known as the

Early effect. This decrease in effective base width has three consequences:

1. There is less chance for recombination within the base region. Hence,  $\alpha$  increases with increasing

$V_{CB}$ .

2. The charge gradient is increased within the base, and consequently, the current of

### 5. Explain output characteristics of CE configuration .(3 marks)

Output Characteristics of CE configuration- To determine the output characteristics, in CE the base current  $I_B$  is kept constant at a suitable value by adjusting the base-emitter voltage,  $V_{BE}$ . The magnitude of the collector-emitter voltage  $V_{CE}$  is increased in suitable equal steps from zero and the collector current  $I_C$  is noted for each setting  $V_{CE}$ . Now, the curves of  $I_C$  versus  $V_{CE}$  are plotted for different constant values of  $I_B$ . The output characteristics thus obtained through the graph.

### 6. In a grounded base configuration , $I_C$ is 0.96 mA and base current is 50uA.calculate alpha and beta

- ☐ 0.99 and 20
- ☒ 0.95 and 19.2
- ☐ 0.95 and 20
- ☐ 0.99 and 18

### 7. IN CB arrangement ,a voltage drop of 5V is obtained across load 5Kohm, connected in collector circuit. If alpha is 0.99,find $I_C$ and $I_B$ .

- ☐ 1mA and 0.1mA
- ☐ 1.2 mA and 1mA
- ☒ 1mA and 0.01mA
- ☐ Other

8. In CE transistor,  $V_{ce}$  changes from 5V to 10 V, causes the change in collector current from 5 mA to 5.8 mA. Determine dynamic output resistance.

☒ 6.25mA

☐ 5.5mA

☐ 6mA

☐ Other

9. In a CE transistor, at  $V_{ce}$  of 1 V,  $V_{be}$  is adjusted to give a collector current of 1 mA. Keeping  $V_{be}$  constant,  $V_{ce}$  is increased to 11 V. Find the new value of  $I_c$  if the early voltage  $V_a$  is 100V.

☒ 1.1mA

☐ 2mA

☐ 1 mA

☐ Other

☐ Send me an email receipt of my responses

Submit

This content is created by the owner of the form. The data you submit will be sent to the form owner. Microsoft is not responsible for the privacy or security practices of its customers, including those of this form owner. Never give out your password.

Powered by Microsoft Forms | [Privacy and cookies](#) | [Terms of use](#)